
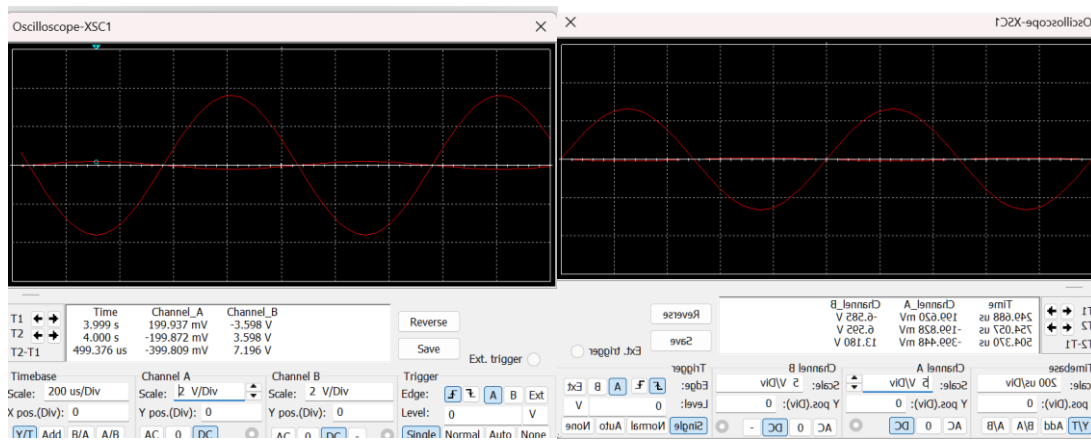


Logbook

Inverting op-amp

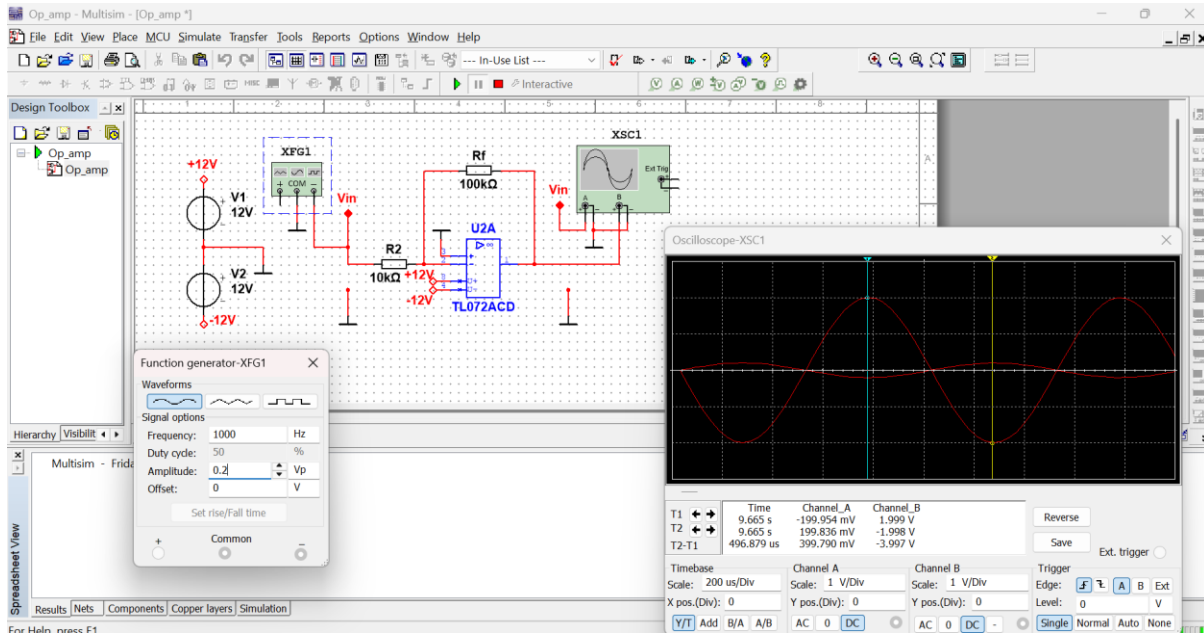- Gain $A = -10$
- Amplitude CH0 = 400 mV
- Amplitude CH1 = -4V



Non-Inverting Op-amp

- Gain $A = 11$
- Amplitude CH0 = -400mV
- Amplitude CH1 = -4.4V

