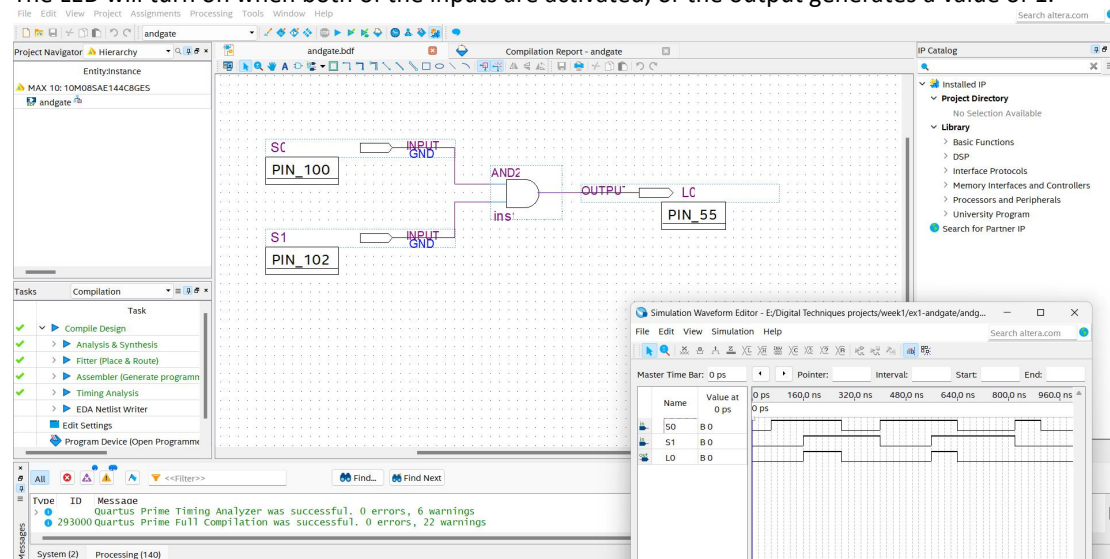


Exercise 1:

The LED will turn on when both of the inputs are activated, or the output generates a value of 1.




Exercise 2:

1. Truth table:

a	b	L
0	0	0
0	1	1
1	0	1
1	1	0

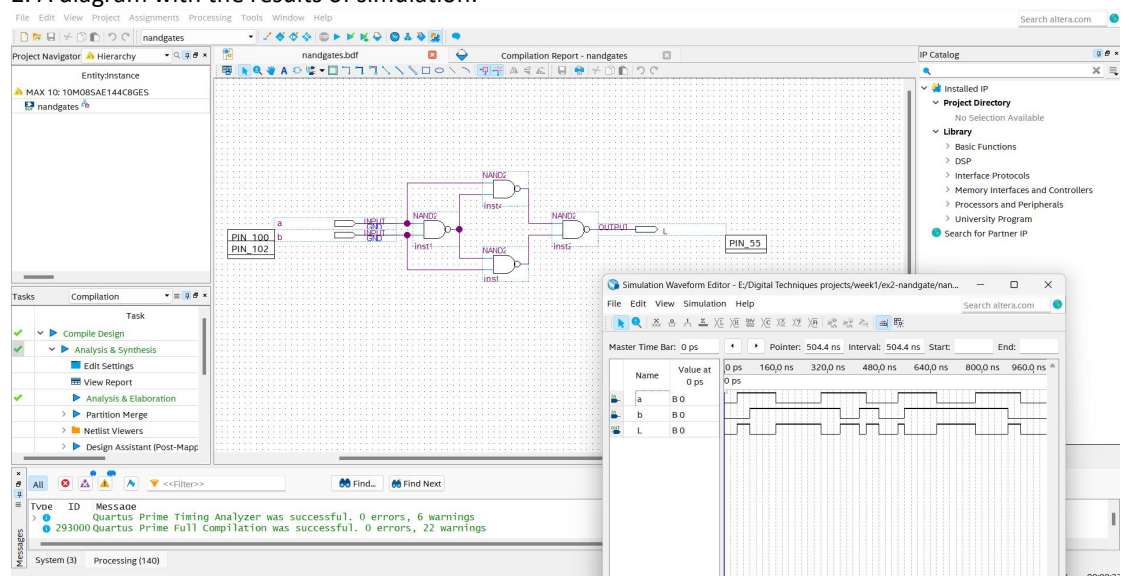2. A diagram with the results of simulation:



3. Which logical operator is realized by the circuit you' ve just built? \rightarrow It's EXOR logical operator.