
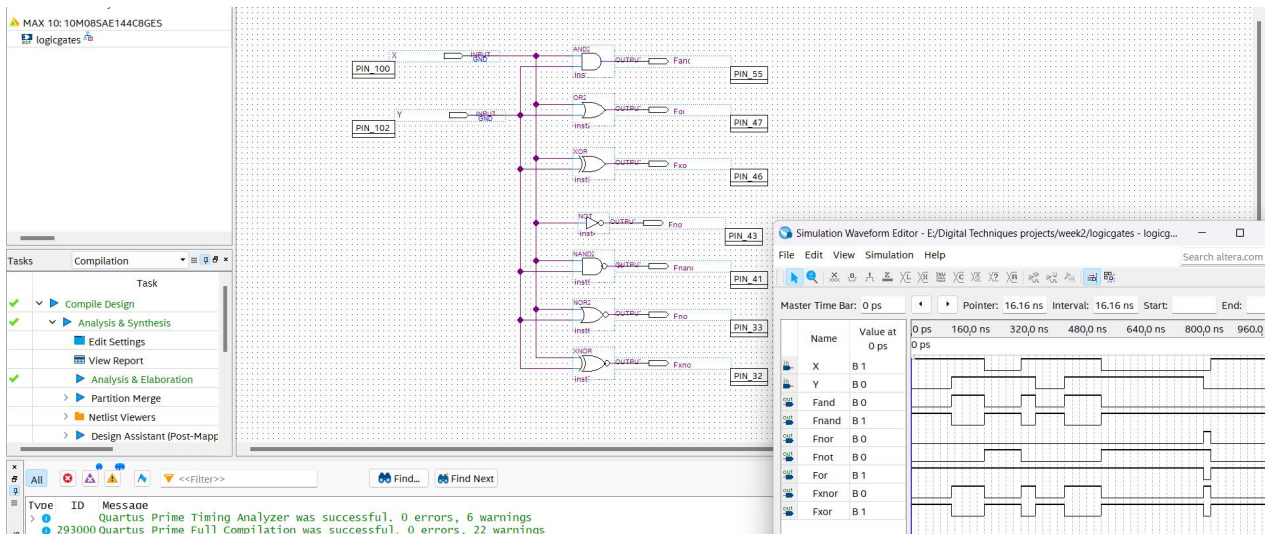


Exercise 1:

X	Y	AND	OR	XOR	NOT	NAND	NOR	XNOR
0	0	0	0	0	1	1	1	1
0	1	0	1	1	1	1	0	0
1	0	0	1	1	0	1	0	0
1	1	1	1	0	0	0	0	1

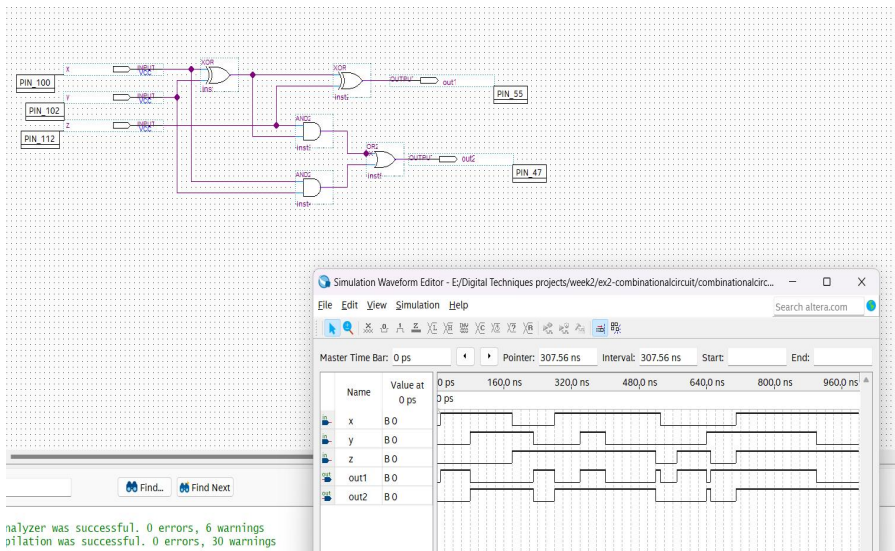

Exercise2:



x	y	z	Out1	Out2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

The circuit shows that if 1 of the 3 inputs is true, then output1 will be activated. If 2 of them are true, then output2 will be activated. Also, if all of the 3 inputs are true, then output1 and output2 will be activated.